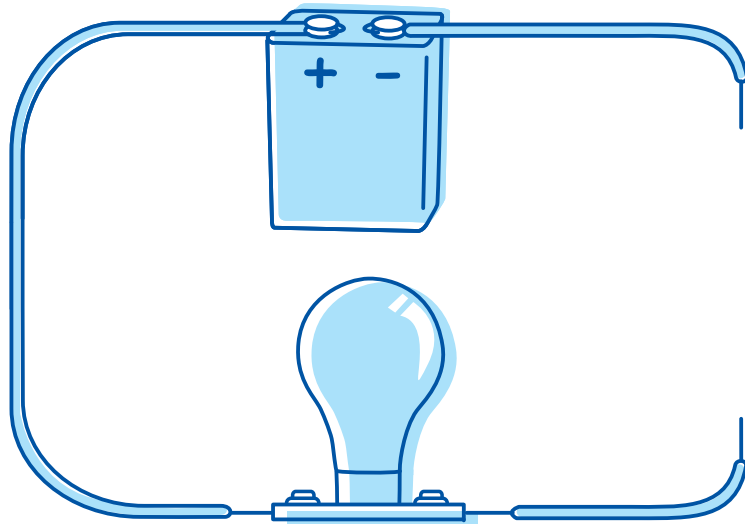


# Electrical Circuits


Electricity needs to flow around a circuit. If there is a break in a circuit it will stop the flow.

Complete these circuits.

1.




2.


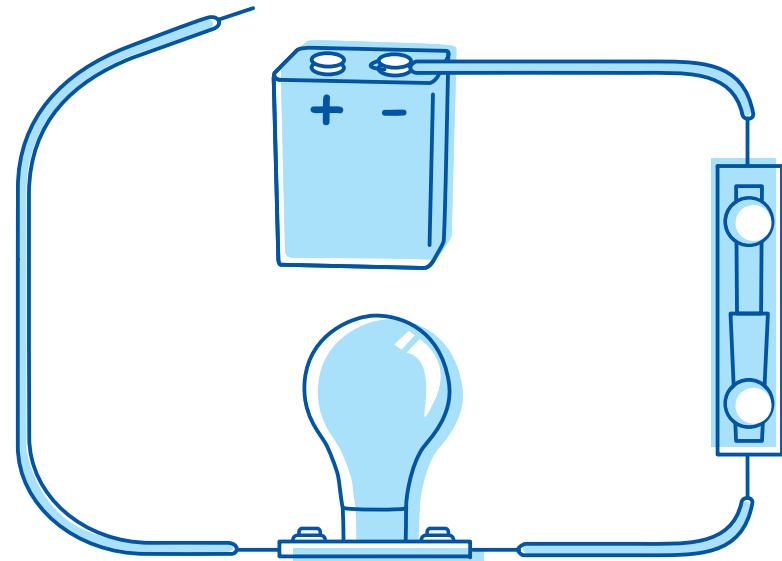


Please remember to recycle this activity

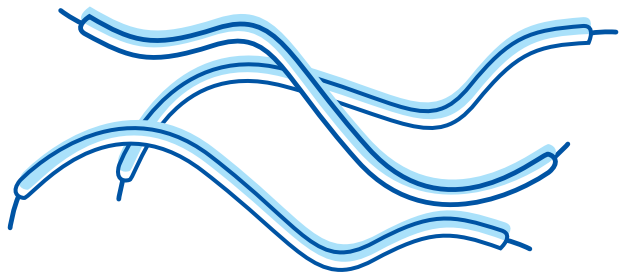Use the items below to make your own circuit.



+

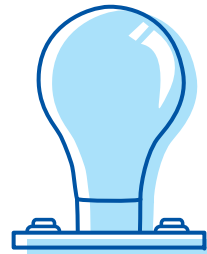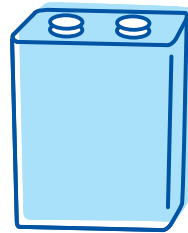

-

