
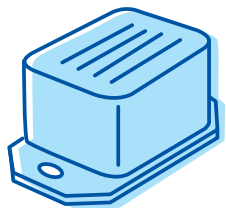
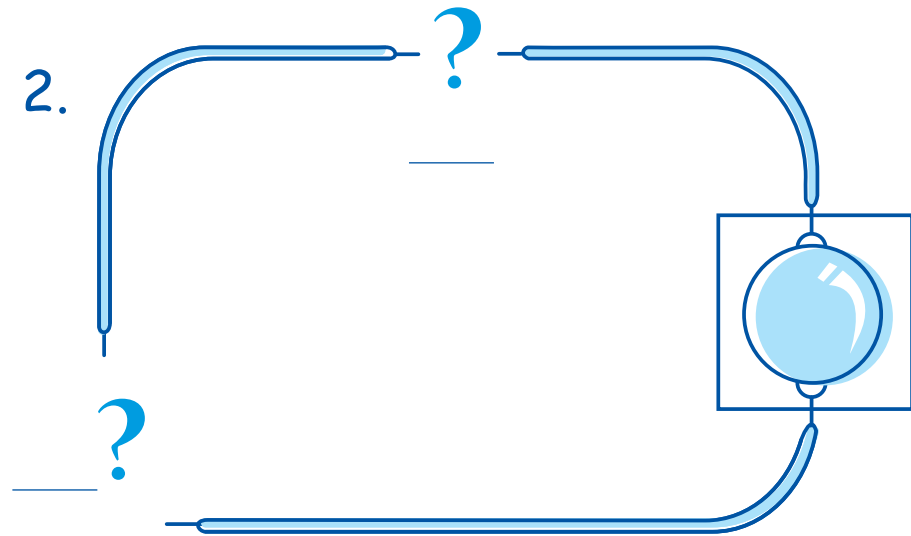


iChild[®].co.uk

Buzz off

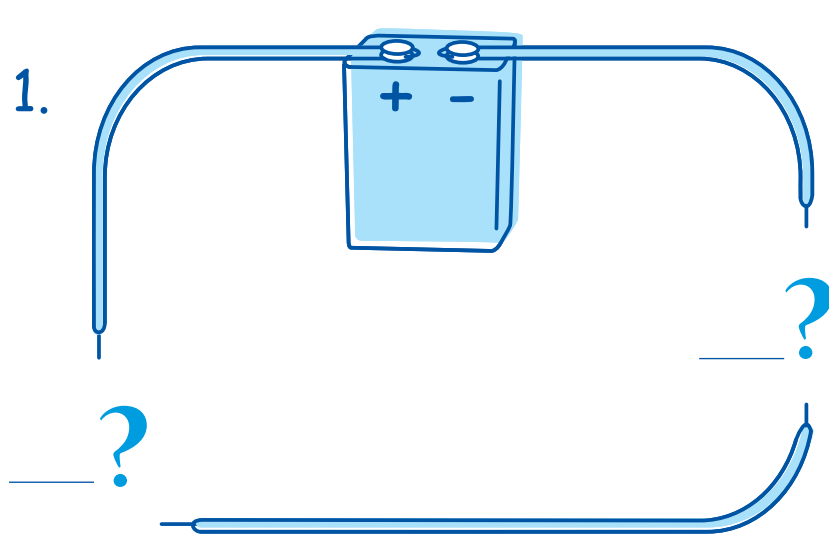
Look at these circuits. See if you can complete them using the things below



A. Buzzer



B. Switch

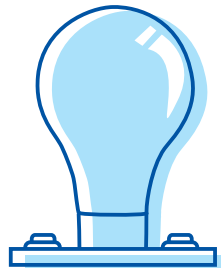


C. Bulb



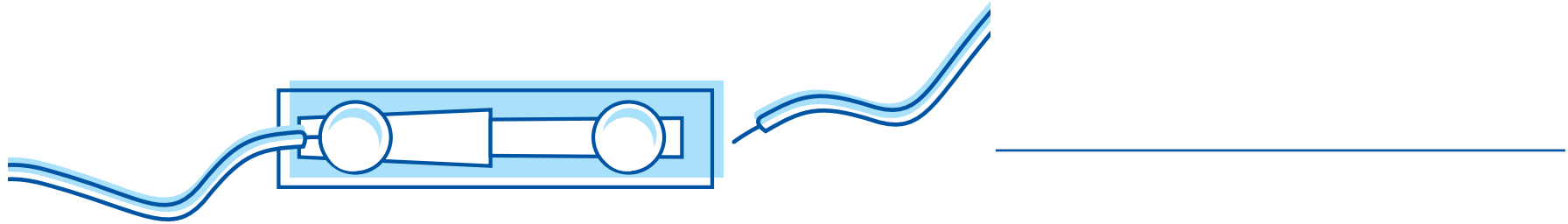D. Battery

Look at this simple switch. What do you think is missing?



Complete these sentences.

1. Batteries should never be taken _____
A. apart B. to school C. on a bus
2. Torches can run on _____
A. batteries B. wood C. air
3. A circuit must be _____ to work.
A. complete B. incomplete C. split
4. As the chemicals get used up in a battery they get _____
A. weaker B. heavier C. stronger
5. _____ can be used for door bells.
A. Buzzers B. Chocolate C. String

