
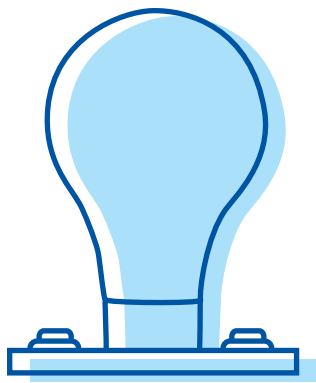


Making a circuit

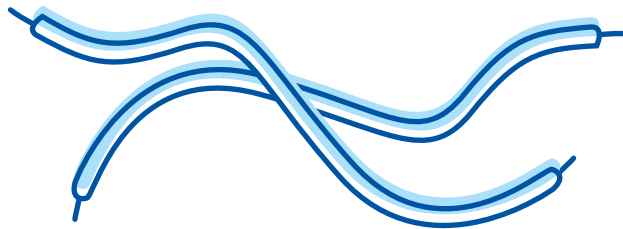To make a light work, you need to make a circuit.
Here is what you will need.



A light bulb
(on board with terminals)



Two pieces of wire



A battery
(with 2 terminals)

On the next page draw how you would fit these things together.



Please remember to recycle this activity

