
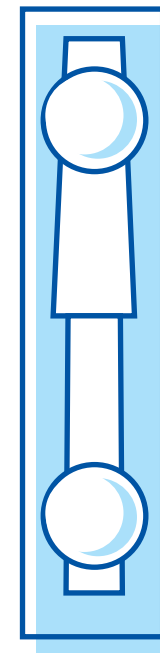


Making a switch

Here is a switch

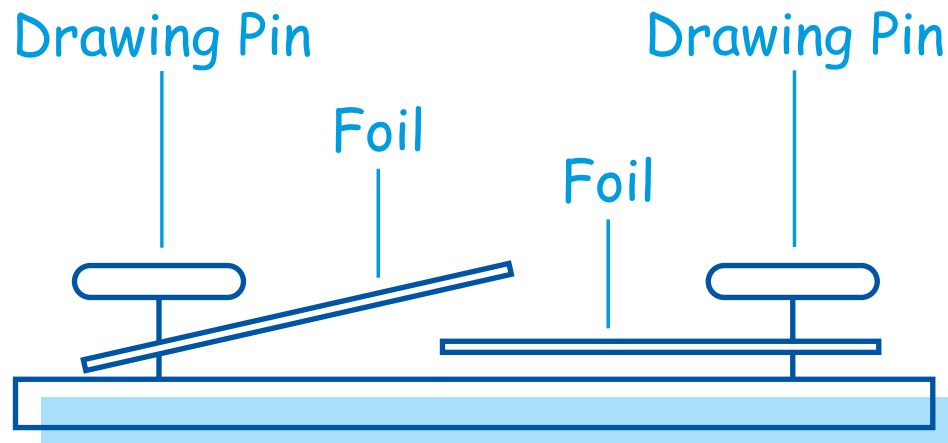

View from
above

Draw another circuit on the page opposite to include your switch. When the wires connect the light will come on.



Please remember to recycle this activity

