

# Symbols and circuits

Certain symbols are used when drawing **electrical circuits**.  
See if you can match the **names** and **symbols**.

## Symbols







LAMP \_\_\_\_\_

BATTERY \_\_\_\_\_

SWITCH \_\_\_\_\_

## Circuits

Complete these circuits.

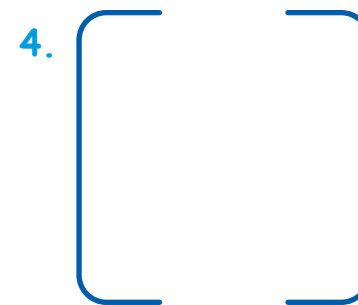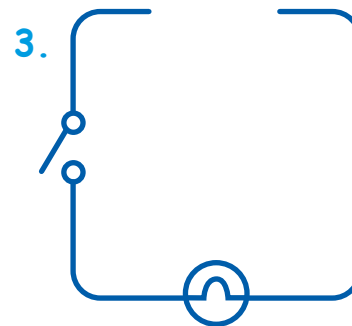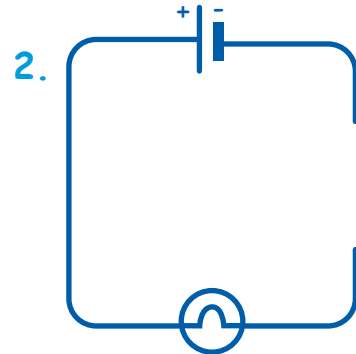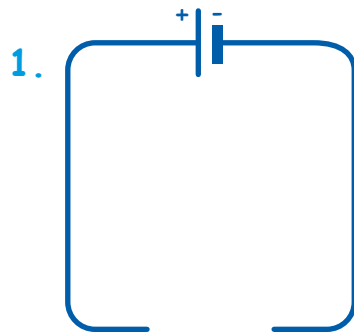

Please remember to recycle this activity